

# EE221 Circuits II


April 17<sup>th</sup>, 2021

## Intro to MATLAB


$L = 15\text{mH}$   $I_L(0) = 0$

$$V_L(s) = V_{in} \frac{R}{R + sL}$$

$$= V_{in} \frac{R/2}{s + R/2}$$

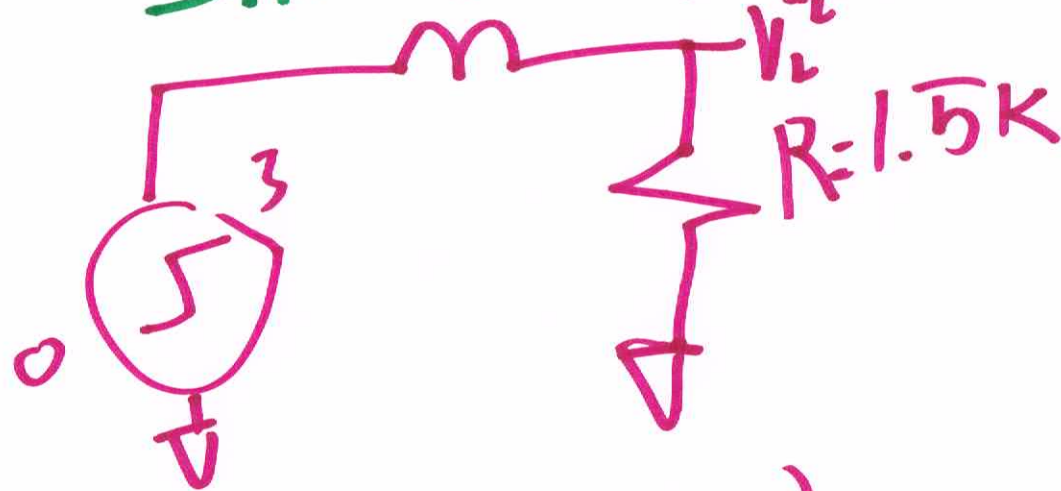

`Pulse(0, 3, 10u, 10u, 10u, 60u)`

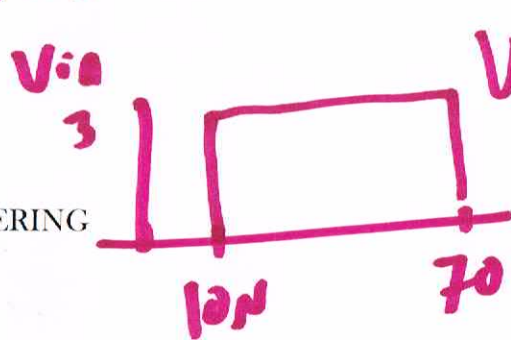

$$V_{in}(t) = 3u(t - 10\mu) - 3u(t - 70\mu)$$

$$= \left[ \frac{3e^{-s10\mu}}{s} - \frac{3e^{-s70\mu}}{s} \right]$$

$$V_L(s) = \frac{R/L}{s + R/L} \left[ \frac{3e^{-s \cdot 10\mu}}{s} - \frac{3e^{-s \cdot 70\mu}}{s} \right]$$

$$= \left[ \frac{A}{s} + \frac{B}{s + R/L} \right] e^{-s \cdot 10\mu} - \left[ \frac{C}{s} + \frac{D}{s + R/L} \right] e^{-s \cdot 70\mu}$$

$$\left\{ \frac{R/L}{0 + R/L} = 3 = A = C \right. \quad \left. \tau = \frac{L}{R} \right.$$

$$= V_L(s) = \left[ \frac{3}{s} - \frac{3}{s + R/L} \right] e^{-s \cdot 10\mu} - \left[ \frac{3}{s} - \frac{3}{s + R/L} \right] e^{-s \cdot 70\mu}$$

$$B = \frac{3 \cdot R/L}{-R/L} = -3 = D$$

$$V_L(t) = \left( 3 - 3e^{-\frac{(t-10\mu)}{\tau}} \right) u(t-10\mu) - \left( 3 - 3e^{-\frac{(t-70\mu)}{\tau}} \right) u(t-70\mu)$$

$$V_m(t) = 3v(t-10\mu) - 3v(t-70\mu)$$

$$V_m(t) - V_u(t) = + 3e^{-\frac{(t-10\mu)}{\tau}} v(t-10\mu) - 3e^{-\frac{(t-10\mu)}{\tau}} v(t-70\mu)$$

---