

Quiz #3 EE 360 Fall 2021

Name: _____

Attempt and grade yourself with a pen

Show your work for credit and place boxes around your answers.

1. Define (in written English):

- A bounded signal

2. Determine a difference equation for the following circuit. Hint: $I_C(t) = C \cdot \frac{dV_{out}(t)}{dt}$

