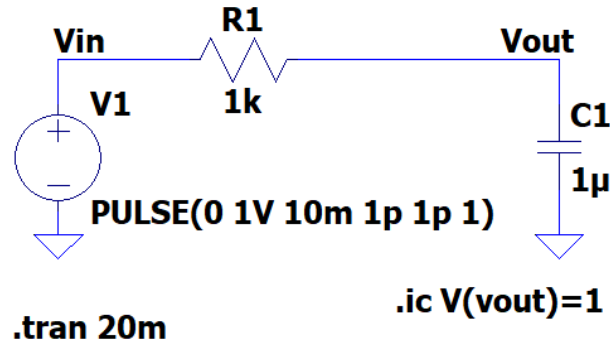


Open book and open notes

**Show your work for credit and place boxes around your answers.**

Consider the following RC circuit



That has an input voltage signal,  $V_{in}(t)$ , output voltage signal,  $V_{out}(t)$ , and an initial voltage at the capacitor of  $V_{out}(t = 0^-) = 1V$ .

1. Describe the system with differential equations. You may replace  $V_{in}(t) = x(t)$  and  $V_{out}(t) = y(t)$  at the end. (hint,  $I_C(t) = C \cdot \frac{dV_{out}(t)}{dt}$ )

2. Convert the differential equation from above using the Laplace Transform (hint: use the unilateral Laplace Transform property of differentiation). Identify the zero-input and zero-state responses. Sketch the region of convergence.

3. Solve for the total response of the system when the input is  $V_{in}(t) = 1V \cdot u(t - 10ms)$ . (hint: solve for the ZIR and ZSR of the system from problem 2). Verify in LTSpice.