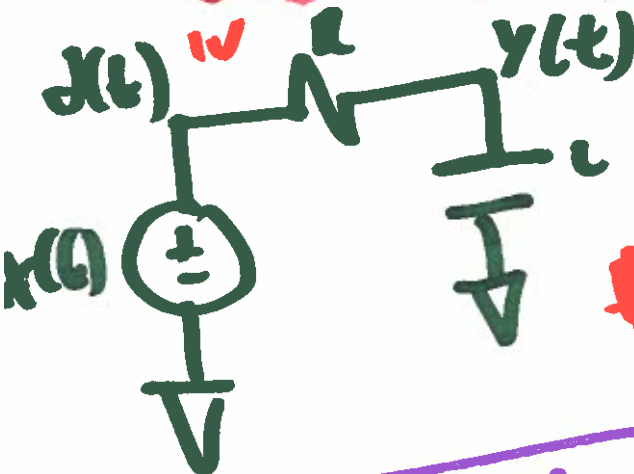


The Laplace Transform

Practical! SS equations

Wed. November 10th, 2021



$$\frac{dy(t)}{dt} + \frac{1}{RC} y(t) = \frac{1}{RC} x(t)$$

$s_{\text{zoo}} = -\frac{1}{RC}$

$$L(s) \left[s^2 y(s) + a_1 y(s) + y(s) \right] = b_1 s x(s) + b_0 x(s)$$

HW: $d_{a2} \ddot{y} + a_1 \dot{y} + a_0 y = b_1 \dot{x} + b_0 x \Rightarrow$

1) $d^n x/dt^n \rightarrow s^n Y(s) - s^{n-1} y(t=0) - \dots - s^{n-1} \frac{dy^{(n-1)}(t=0)}{dt^{n-1}}$

Memorize!

I.C.

$H(s) = \frac{Y(s)}{X(s)}$

General RC Filter TF

Res $\frac{1}{RC}$


Spole $= -\frac{1}{RC} = -1K$

$$H(s) = \frac{1}{1 + sRC} = \frac{1}{s + \frac{1}{RC}}$$

$[s + \frac{1}{RC}]$ pole $= -\frac{1}{RC}$

$\tau = 1ms$

Pole Location!

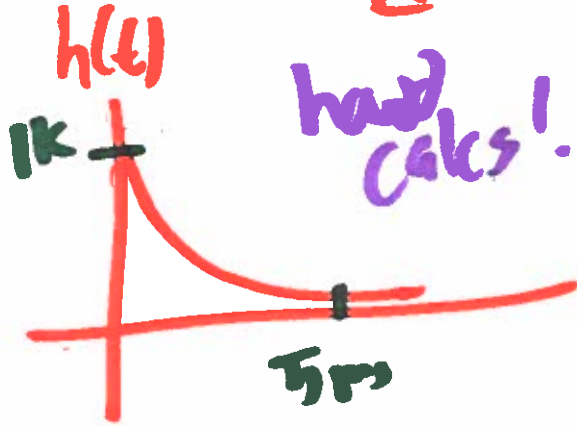


hard calcs!

$$\mathcal{L}^{-1}\{H(s)\} = \frac{1}{RC} e^{-\frac{1}{RC}t}$$


$$1K e^{-\frac{t}{1ms}}$$

2)

State Space Eqns.

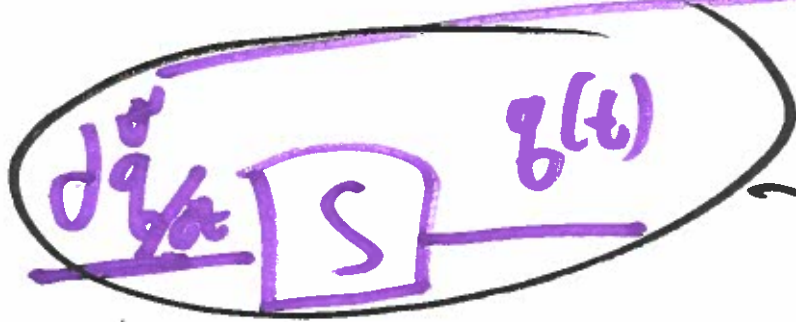

from Ch. 2/3?

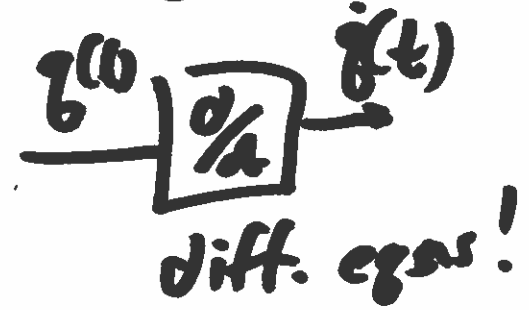


$$\int \frac{dy(t)}{dt} + \int \frac{1}{rc} y(t) = \int \frac{1}{rc} x(t)$$

$$y(t) + \frac{1}{rc} Sy = \frac{1}{rc} Sx$$

$$y(t) = \frac{1}{rc} Sx - \frac{1}{rc} Sy$$

DFII:

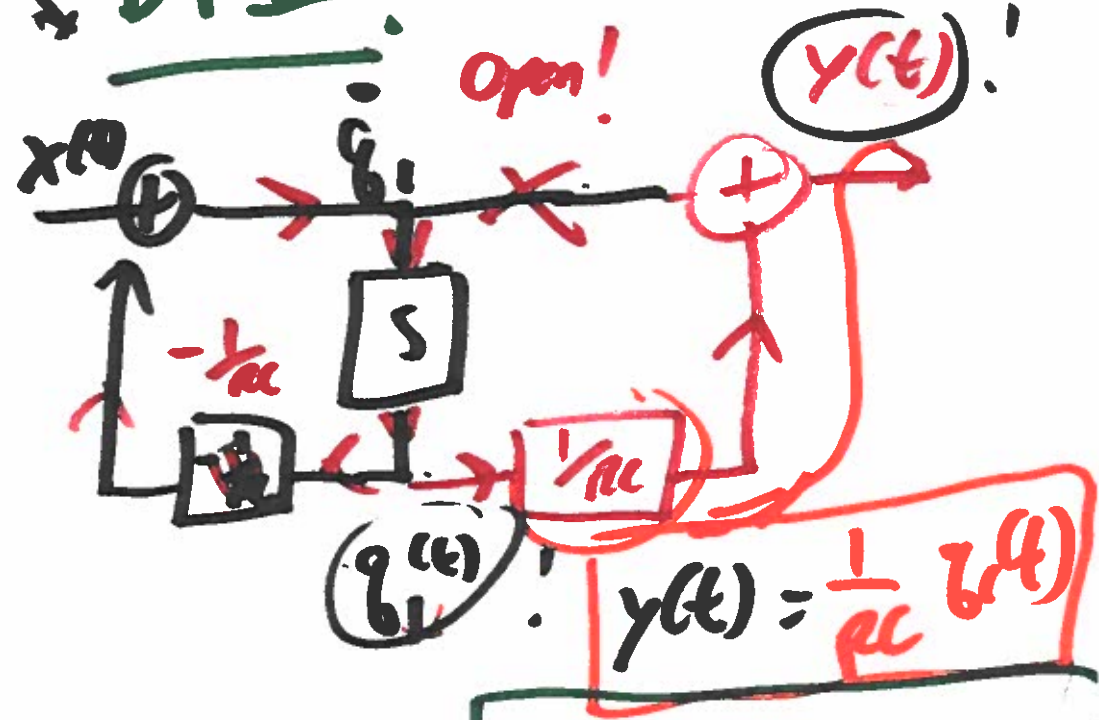

Open!

y(t)

$$y(t) = \frac{1}{rc} i(t)$$

$$i(t) = x(t) - \frac{1}{rc} i(t)$$

ss eqns:

$$\dot{q} = Aq + Dx$$

$$y = Cq + Dx$$

3)

$$\dot{q} = [q, \omega] = \begin{bmatrix} -1/\tau_c \\ 1/\tau_c \end{bmatrix} [q_1^0] + [1] x(t)$$

$$y = [y(t)] = \begin{bmatrix} 1/\tau_c \end{bmatrix} [q, \omega] + 0$$

← EE 370!
freq!

SS. Eqs!

use Controls Toolbox!

$$H(s) = \frac{1}{\tau_c (s + 1/\tau_c)}$$

$s = j\omega$
 $\omega = 2\pi F \rightarrow F = \frac{\omega}{2\pi}$


10 Hz
-Sub

$$y(t) = h(t) * x(t)$$

$x = e$

10 Hz
-Sub + $\angle H(s=s_0)$

$$y(t) = \left| H(s=s_0) \right| e^{j\omega t + \angle H(s=s_0)}$$

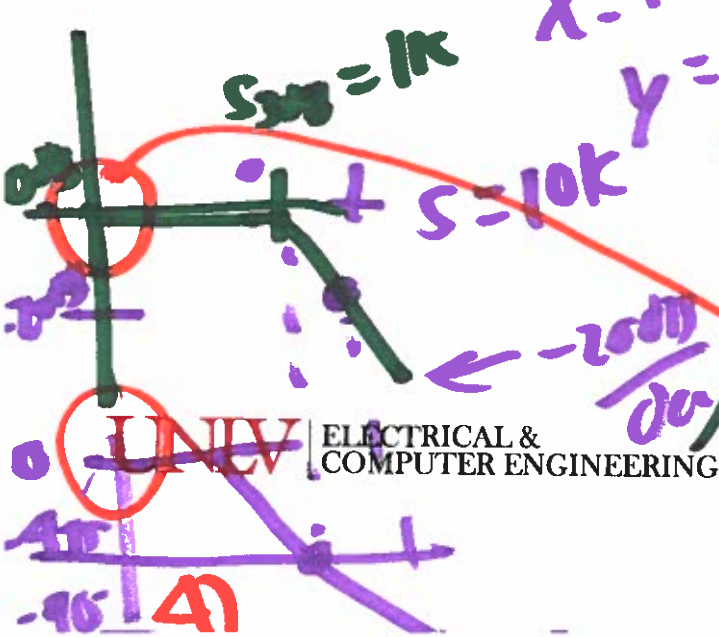

10 Hz
-Sub + \angle
 $x = 1V e^{j\omega t}$
 $y = 0.1V e^{j\omega t + \phi}$

$s = DC = 0!$

$$y(t) = |H(s=0)| e^{j\omega t + \angle H(s=0)}$$

$= |1V|!$
 $\phi = 0!$

DC Gain of RC Filter = 1!

DC Gain!

$$H(s) = \frac{1}{RC} \frac{1}{s + \frac{1}{RC}}$$

$$H(s=0) = \frac{1}{RC} \frac{1}{0 + \frac{1}{RC}} = RC \left(0 + \frac{1}{RC}\right) = 1$$

$$1$$

$$Y(s) = H(s) X(s)$$

$U(s) \rightarrow u(t)$!
Step Response!

$$U(s) = \frac{1}{s}$$

$p_k = 0$

$$Y(s) = H(s) U(s)$$

$$Y(s) = H(s) \cdot \frac{1}{s}$$

$$= \frac{1}{RC} \left(\frac{1}{s + \frac{1}{RC}} - \frac{1}{s} \right) = \frac{A}{s} + \frac{B}{s + \frac{1}{RC}}$$

check for stability
- Damping factor
- Set. time, etc.

Heaviside
Theorem:

$$A = \left. H(s) X(s) \right|_{s=0} = \left. \frac{1}{RC} \frac{1}{s} \right|_{s=0} = \frac{1}{RC} \cdot \frac{1}{0} = \frac{1}{RC} \cdot \infty = \infty$$

$$\beta = \left. \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}} \cdot \frac{1}{s} \right|_{s = -\frac{1}{RC}} = \frac{1}{RC} \cdot \frac{1}{s} = \frac{-RC}{RC} = \boxed{-1}$$


$$s = -\frac{1}{RC}$$

Asymptote stable!
 $Res = 1$
 $pole = -\frac{1}{RC}$

Step Response:

$$Y(s) = \frac{1}{s} - \frac{1}{s + \frac{1}{RC}}$$
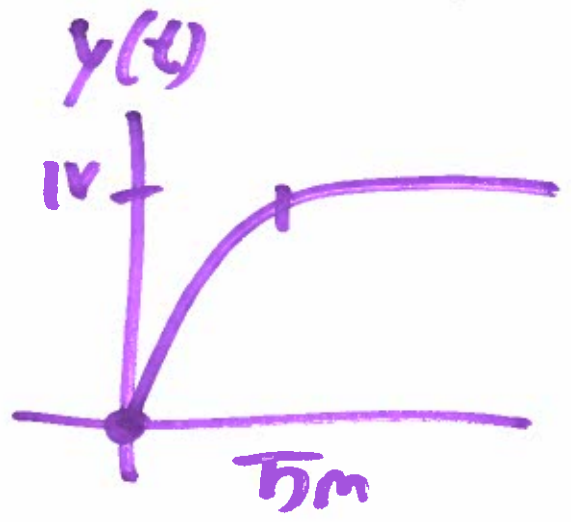
$$y(t) = \underline{v(t)} - 1 e^{(-\frac{1}{RC})t} \underline{v(t)}$$



$$y(t) = [1 - e^{-\frac{t}{RC}}] v(t)$$

6)