

Class:	CPE300L		Semester:	Fall 2021
Points		Document author:	Jerrod Batu	
		Author's email:	batuj1@unlv.nevada.edu	
		Document topic:	Postlab 3	
Instructor's comments:				

1. Introduction / Theory of Operation

Throughout this lab, I will learn about Quartus, VCS, and continue my knowledge of Verilog HDL. Specifically, I will have a better understanding of VCS for testbenches and combinational circuit designs. This lab will include a 7-segment in Verilog, magnitude comparators, ripple adder, and simple ALUS.

1. **Megafunction** in Quartus are ready-made, pre-tested practical blocks of code that expand existing design procedures. They decrease design assignments, extremely shorten tasks, and allow designers to optimize their time and energy on improving their system-level items and existing intellectual properties. Altera provides a library of megafunctions necessary to design more efficient logic synthesis and device applications.
2. The MegaWizard Plug-In Manager, provides several **applications** of custom megafunction variations to include in a design file. The main goal of these applications is to lessen the amount of instructions when instantiating specific functions. Some of these applications include: altfp_abs, altfp_add_sub, lpm_divide, lpm_and, lpm_or, etc.
 - altfp_abs: floating-point absolute value megafunction
 - altfp_add_sub: floating-point adder/subtractor megafunction
 - lpm_divide: parameterized divider megafunction
 - lpm_and: parameterized AND gate megafunction
 - lpm_or: parameterized OR gate megafunction

2. Prelab

https://docs.google.com/document/d/10xN_bbupBwU2bnhr079n2DhvzONp04eo/edit?usp=sharing&oid=102808507017671072128&rtpof=true&sd=true

This is the link to my prelab 3.

3. Results of Experiments


Experiment 1

a.


```
1  module seg7 (data,segments);
2      input [3:0] data;
3      output reg [6:0] segments;
4      always @ (data) begin
5          case (data)
6              0 : segments = 7'b0000001;
7              1 : segments = 7'b1001111;
8              2 : segments = 7'b0010010;
9              3 : segments = 7'b0000110;
10             4 : segments = 7'b1001100;
11             5 : segments = 7'b0100100;
12             6 : segments = 7'b0100000;
13             7 : segments = 7'b0001111;
14             8 : segments = 7'b0000000;
15             9 : segments = 7'b0000100;
16             10: segments = 7'b0001000;
17             11: segments = 7'b1100000;
18             12: segments = 7'b0110001;
19             13: segments = 7'b1000010;
20             14: segments = 7'b0110000;
21             15: segments = 7'b0111000;
22             default: segments = 7'b1111111;
23         endcase
24     end
25 endmodule
26
```

This is my Verilog code for a 7-segment display.


b.

 

 
This is my DE2 board showing the 7-segment display of “0” when the data input is 0000.



 This is my DE2 board showing the 7-segment display of "7" when the data input is 0111.



 This is my DE2 board showing the 7-segment display of "C" when the data input is 1100.



This is my DE2 board showing the 7-segment display of "F" when the data input is 1111.

Experiment 2

a.

```
1  module magCompare (a,b,gt,eq,lt);
2      input a,b;
3      output reg gt,eq,lt;
4
5      always @ (a,b) begin
6          gt = (a > b) ? 1 : 0; // greater than
7          eq = (a == b) ? 1 : 0; // equal to
8          lt = (a < b) ? 1 : 0; // less than
9      end
10 endmodule
11
12 //magCompareTB testbench
13 module magCompareTB;
14     parameter N = 4;
15     reg a_tb;
16     reg b_tb;
17     wire gt_tb;
18     wire eq_tb;
19     wire lt_tb;
20     reg [0:N] a_tb_array;
21     reg [0:N] b_tb_array;
22     reg [0:N] gt_tb_array;
23     reg [0:N] eq_tb_array;
24     reg [0:N] lt_tb_array;
25
26     magCompare U0 (
27         .a (a_tb),
28         .b (b_tb),
29         .gt (gt_tb),
30         .eq (eq_tb),
31         .lt (lt_tb)
32     );
33
34     initial begin
35         $display("\t\ttime\ta_tb,\tb_tb,\tgt_tb,\teq_tb,\tlt_tb");
36         $monitor("%d,\t%b,\t%b,\t%b,\t%b,\t%b", $time, a_tb, b_tb, gt_tb, eq_tb, lt_tb);
37     end
38
39     initial begin
40         //initialization of input and output arrays
41         a_tb_array [0] = 0;
42         b_tb_array [0] = 0;
43         gt_tb_array [0] = 0;
44         eq_tb_array [0] = 1;
45         lt_tb_array [0] = 0;
46         #10
47         a_tb_array [1] = 0;
48         b_tb_array [1] = 1;
49         gt_tb_array [1] = 0;
50         eq_tb_array [1] = 0;
51         lt_tb_array [1] = 1;
52         #10
53         a_tb_array [2] = 1;
54         b_tb_array [2] = 0;
55         gt_tb_array [2] = 1;
56         eq_tb_array [2] = 0;
57         lt_tb_array [2] = 0;
```


```

58     #10
59     a_tb_array [3] = 1;
60     b_tb_array [3] = 1;
61     gt_tb_array [3] = 0;
62     eq_tb_array [3] = 1;
63     lt_tb_array [3] = 0;
64     #10
65     a_tb_array [4] = 0;
66     b_tb_array [4] = 0;
67     gt_tb_array [4] = 0;
68     eq_tb_array [4] = 1;
69     lt_tb_array [4] = 0;
70 end
71
72 integer i;
73 always begin
74     for (i = 0; i <= N ; i = i + 1) begin
75         a_tb <= a_tb_array [i];
76         b_tb <= b_tb_array [i];
77         #100;
78     end
79     $display("\t\t\tTest Finished");
80     $stop;
81 end
82 endmodule
83

```

This is my Verilog code for the magnitude comparator testbench from prelab 3.

b.

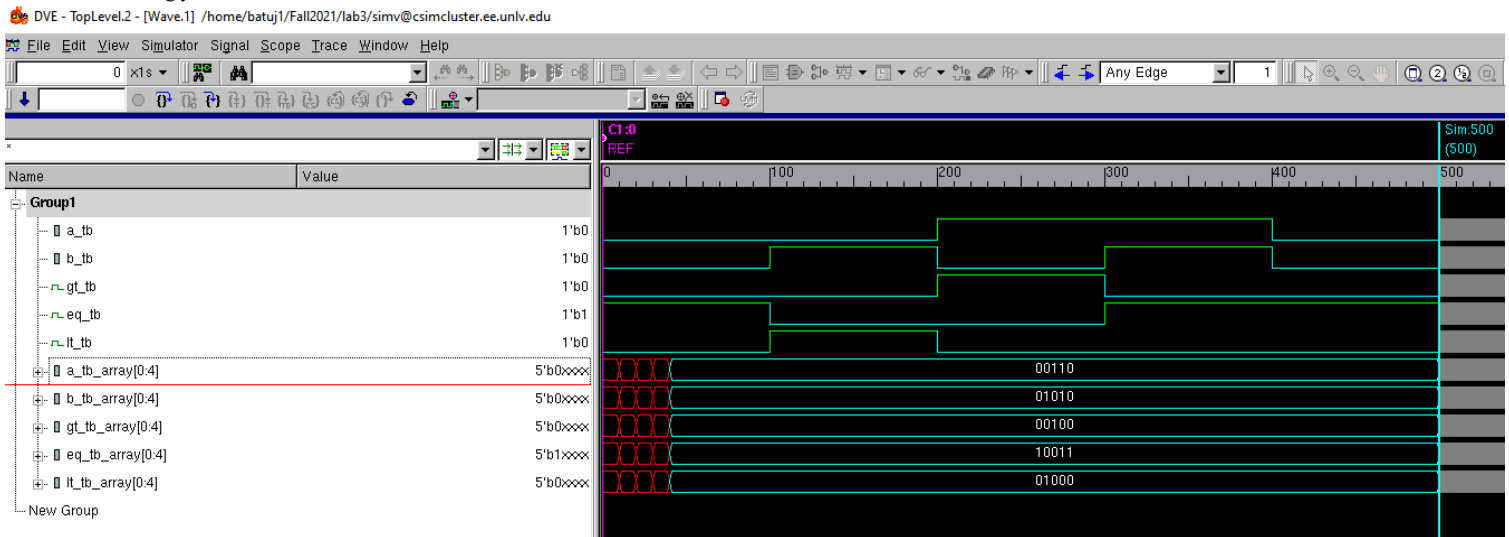

These are my VCS waveforms for the magnitude comparator testbench. The red waveforms represent the beginning delays at the start of the code.


Chronologic VCS simulator copyright 1991-2017
Contains Synopsys proprietary information.
Compiler version N-2017.12-SP2-14; Runtime version N-2017.12-SP2-14; Sep 14 13:49 2021
VCD+ Writer N-2017.12-SP2-14 Copyright (c) 1991-2017 by Synopsys Inc.
The file '/home/batuj1/Fall2021/lab3/inter.vpd' was opened successfully.

time	a_tb,	b_tb,	gt_tb,	eq_tb,	lt_tb
0,	0,	0,	0,	1,	0
100,	0,	1,	0,	0,	1
200,	1,	0,	1,	0,	0
300,	1,	1,	0,	1,	0
400,	0,	0,	0,	1,	0


Test Finished

This is the console output from VCS including the time, inputs, and results of the magnitude comparator testbench.


c.

 

 
This is the DE2 board implementation of the magnitude comparator when $a > b$ as $a = 1$ and $b = 0$.



 This is the DE2 board implementation of the magnitude comparator when $a < b$ as $a = 0$ and $b = 1$.



 This is the DE2 board implementation of the magnitude comparator when $a = b$ as $a = 1$ and $b = 1$.



This is the DE2 board implementation of the magnitude comparator when $a = b$ as $a = 0$ and $b = 0$.

Experiment 3

a.

```
1 //4-bit Ripple Carry Adder
2 module rippleAdd (A, B, Cinra, Coutra, Sumra, Segments);
3     input [3:0] A, B;
4     input Cinra;
5     output [3:0] Sumra;
6     output Coutra;
7     output reg [6:0] Segments;
8     wire [3:1] carry;
9
10    //instantiate four copies of the FullAdder
11    FullAdd FA0 (A[0],B[0],Cinra,Sumra[0],carry[1]);
12    FullAdd FA1 (A[1],B[1],carry[1],Sumra[1],carry[2]);
13    FullAdd FA2 (A[2],B[2],carry[2],Sumra[2],carry[3]);
14    FullAdd FA3 (A[3],B[3],carry[3],Sumra[3],Coutra);
15
16    //7segment display
17    always @ (Sumra) begin
18        case (Sumra)
19            0 : Segments = 7'b0000001;
20            1 : Segments = 7'b1001111;
21            2 : Segments = 7'b0010010;
22            3 : Segments = 7'b0000110;
23            4 : Segments = 7'b1001100;
24            5 : Segments = 7'b0100100;
25            6 : Segments = 7'b0100000;
26            7 : Segments = 7'b0001111;
27            8 : Segments = 7'b0000000;
28            9 : Segments = 7'b0000100;
29            10: Segments = 7'b0001000;
30            11: Segments = 7'b1100000;
31            12: Segments = 7'b0110001;
32            13: Segments = 7'b1000010;
33            14: Segments = 7'b0110000;
34            15: Segments = 7'b0111000;
35            default: Segments = 7'b1111111;
36        endcase
37    end
38 endmodule
39
40
41 //1-bit Full Adder
42 module FullAdd (X,Y,Cinfa,Sumfa,Coutfa);
43     input X, Y, Cinfa;
44     output Sumfa, Coutfa;
45
46     assign Sumfa = X ^ Y ^ Cinfa;
47     assign Coutfa = (X && Y) || ((X^Y) && Cinfa);
48 endmodule
49
```

This is my Verilog code for implementing a Full Adder module into a 4-bit Ripple Carry Adder including the 7-segment output display.

b.

```
1  `timescale 1 ns / 100 ps
2
3  //4-bit Ripple Carry Adder
4  module rippleAdd (A, B, Cinra, Coutra, Sumra, Segments);
5      input [3:0] A, B;
6      input Cinra;
7      output [3:0] Sumra;
8      output Coutra;
9      output reg [6:0] Segments;
10     wire [3:1] carry;
11
12     //instantiate four copies of the FullAdder
13     FullAdd FA0 (A[0],B[0],Cinra,Sumra[0],carry[1]);
14     FullAdd FA1 (A[1],B[1],carry[1],Sumra[1],carry[2]);
15     FullAdd FA2 (A[2],B[2],carry[2],Sumra[2],carry[3]);
16     FullAdd FA3 (A[3],B[3],carry[3],Sumra[3],Coutra);
17
18     //7segment display
19     always @ (Sumra) begin
20         case (Sumra)
21             0 : Segments = 7'b0000001;
22             1 : Segments = 7'b1001111;
23             2 : Segments = 7'b0010010;
24             3 : Segments = 7'b0000110;
25             4 : Segments = 7'b1001100;
26             5 : Segments = 7'b0100100;
27             6 : Segments = 7'b0100000;
28             7 : Segments = 7'b0001111;
29             8 : Segments = 7'b0000000;
30             9 : Segments = 7'b0000100;
31             10: Segments = 7'b0001000;
32             11: Segments = 7'b1100000;
33             12: Segments = 7'b0110001;
34             13: Segments = 7'b1000010;
35             14: Segments = 7'b0110000;
36             15: Segments = 7'b0111000;
37             default: Segments = 7'b1111111;
38         endcase
39     end
40 endmodule
41
42
43 //1-bit Full Adder
44 module FullAdd (X,Y,Cinfa,Sumfa,Coutfa);
45     input X, Y, Cinfa;
46     output Sumfa, Coutfa;
47
48     assign Sumfa = X ^ Y ^ Cinfa;
49     assign Coutfa = (X && Y) || ((X^Y) && Cinfa);
50 endmodule
51
52
53 //4-bit Ripple Carry Adder TestBench
54 module rippleAddTB;
55     parameter N = 32; //16 tests
56     reg [3:0] A_tb;
57     reg [3:0] B_tb;
```


```

58     reg     Cin_tb;
59     wire [3:0] Sum_tb;
60     wire     Cout_tb;
61     wire [6:0] Seg_tb;
62
63     rippleAdd U0 (
64         .A (A_tb),
65         .B (B_tb),
66         .Cinra (Cin_tb),
67         .Sumra (Sum_tb),
68         .Coutra (Cout_tb),
69         .Segments (Seg_tb)
70     );
71
72     initial begin
73         $display("\t\ttime\tA_tb,\tB_tb,\tCin_tb,\tSum_tb,\tCout_tb,\tSeg_tb");
74         $monitor("%d,\t%b,\t%b,\t%b,\t%b,\t%b", $time, A_tb, B_tb, Cin_tb, Sum_tb, Cout_tb, Seg_tb);
75     end
76
77     integer i;
78     always begin
79         for (i = 0; i <= N; i = i + 1) begin
80             #10;
81             if (i >= 16) begin
82                 A_tb = i;
83                 B_tb = i + 1;
84                 Cin_tb = i - 1;
85             end
86             else begin
87                 A_tb = i;
88                 B_tb = i;
89                 Cin_tb = i;
90             end
91         end
92         $display("\t\tTest Finished");
93         $stop;
94     end
95 endmodule
96
97

```

This is my Verilog code for the 4-bit Ripple Carry Adder testbench including the 7-segment output display.

C.

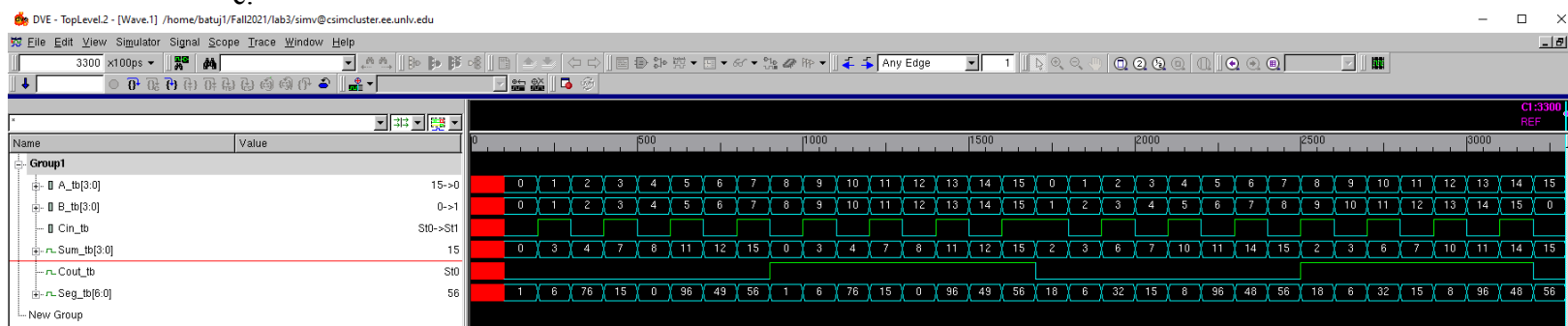

These are my waveforms from VCS that display the inputs and outputs of the 4-bit Ripple Carry Adder testbench including the 7-segment output display. The blocks of red lines indicate delay.


```

Type: [Filter] Severity: [Filter] Code: All
Contains Synopsys proprietary information.
Compiler version N-2017.12-SP2-14; Runtime version N-2017.12-SP2-14; Sep 18 11:24 2021
VCD+ Writer N-2017.12-SP2-14 Copyright (c) 1991-2017 by Synopsys Inc.
The file '/home/batuj1/Fall2021/lab3/inter.vpd' was opened successfully.

```

time	A_tb,	B_tb,	Cin_tb,	Sum_tb,	Cout_tb,	Seg_tb
0,	xxxx,	xxxx,	x,	xxxx,	x,	xxxxxxx
10,	0000,	0000,	0,	0000,	0,	0000001
20,	0001,	0001,	1,	0011,	0,	0000110
30,	0010,	0010,	0,	0100,	0,	1001100
40,	0011,	0011,	1,	0111,	0,	0001111
50,	0100,	0100,	0,	1000,	0,	0000000
60,	0101,	0101,	1,	1011,	0,	1100000
70,	0110,	0110,	0,	1100,	0,	0110001
80,	0111,	0111,	1,	1111,	0,	0111000
90,	1000,	1000,	0,	0000,	1,	0000001
100,	1001,	1001,	1,	0011,	1,	0000110
110,	1010,	1010,	0,	0100,	1,	1001100
120,	1011,	1011,	1,	0111,	1,	0001111
130,	1100,	1100,	0,	1000,	1,	0000000
140,	1101,	1101,	1,	1011,	1,	1100000
150,	1110,	1110,	0,	1100,	1,	0110001
160,	1111,	1111,	1,	1111,	1,	0111000
170,	0000,	0001,	1,	0010,	0,	0010010
180,	0001,	0010,	0,	0011,	0,	0000110
190,	0010,	0011,	1,	0110,	0,	0100000
200,	0011,	0100,	0,	0111,	0,	0001111
210,	0100,	0101,	1,	1010,	0,	0001000
220,	0101,	0110,	0,	1011,	0,	1100000
230,	0110,	0111,	1,	1110,	0,	0110000
240,	0111,	1000,	0,	1111,	0,	0111000
250,	1000,	1001,	1,	0010,	1,	0010010
260,	1001,	1010,	0,	0011,	1,	0000110
270,	1010,	1011,	1,	0110,	1,	0100000
280,	1011,	1100,	0,	0111,	1,	0001111
290,	1100,	1101,	1,	1010,	1,	0001000
300,	1101,	1110,	0,	1011,	1,	1100000
310,	1110,	1111,	1,	1110,	1,	0110000
320,	1111,	0000,	0,	1111,	0,	0111000

```

Test Finished


```

This is my console output from VCS that displays the time for the test to finish, the inputs, and the outputs for the 4-bit Ripple Carry Adder testbench including the 7-segment output display.

d.



 This is my DE2 board with the implementation of the 4-bit RCA displaying the output of $3 + 5$ ($0011 + 0101 = 1000$ and no Cout). The 7-segment display shows the addition to be "8", and the LEDs will follow the output of 1000.



This is my DE2 board with the implementation of the 4-bit RCA displaying the output of $8 + 7$ ($1000 + 0111 = 1111$ and no Cout). The 7-segment display shows the addition to be "F", and the LEDs will follow the output of 1111.



This is my DE2 board with the implementation of the 4-bit RCA displaying the output of $15 + 1$ ($1111 + 0001 = 0000$ and 1 Cout). The 7-segment display shows the addition to be “0” because the addition goes out of the bit range, and the LEDs will follow the output of 0000 with LEDR5 as the Cout.



This is my DE2 board with the implementation of the 4-bit RCA displaying the output of $11 + 11$ ($1011 + 1011 = 0110$ and 1 Cout). The 7-segment display shows the addition to be “6” because the addition goes out of the bit range, and the LEDs will follow the output of 0110 with LEDR5 as the Cout.

Experiment 4

a.

```
1 //simpleALU
2 module simpleALU (A, B, Cin, Cntrl, O, Cout,segments);
3   input [3:0] A,B;
4   input [2:0] Cntrl;
5   input Cin;
6   output reg [3:0] O;
7   output reg Cout;
8   output reg [6:0] segments;
9
10  reg [3:0] Carry, Borrow;
11  always @ (*)
12  begin
13      case(Cntrl)
14          3'b000: begin //INC
15              O = A + 1;
16              if (A == 4'b1111)
17                  begin
18                      Cout = 1;
19                  end
20              else
21                  begin
22                      Cout = 0;
23                  end
24          end
25          3'b001: begin //DEC
26              O = A - 1;
27              Cout = 0;
28          end
29          3'b010: begin //ROR
30              O = {A[0],A[3],A[2],A[1]};
31              Cout = 0;
32          end
33          3'b011: begin //SHR
34              O = A >> 1;
35              Cout = 0;
36          end
37          3'b100: begin //AND
38              O = A & B;
39              Cout = 0;
40          end
41          3'b101: begin //OR
42              O = A | B;
43              Cout = 0;
44          end
45          3'b110: begin //ADD
46              O = A + B + Cin;
47              Carry = (A && B) || ((A && Cin) || (B && Cin));
48              Cout = Carry;
49          end
50          3'b111: begin //SUB
51              O = A - B - Cin;
52              Borrow = (!A && (B ^ Cin)) || (B && Cin);
53              Cout = Borrow;
54          end
55      endcase
56  end
57
```

```
//7-Segment Display
always @ (O) begin
    case (O)
        0 : segments = 7'b0000001;
        1 : segments = 7'b1001111;
        2 : segments = 7'b0010010;
        3 : segments = 7'b0000110;
        4 : segments = 7'b1001100;
        5 : segments = 7'b0100100;
        6 : segments = 7'b0100000;
        7 : segments = 7'b0001111;
        8 : segments = 7'b0000000;
        9 : segments = 7'b0000100;
        10 : segments = 7'b0001000;
        11 : segments = 7'b1100000;
        12 : segments = 7'b0110001;
        13 : segments = 7'b1000010;
        14 : segments = 7'b0110000;
        15 : segments = 7'b0111000;
        default: segments = 7'b1111111;
    endcase
end
odule
```

This is my Verilog code for implementing a 4-bit ALU module including the 7-segment output display.

b.

```
1  `timescale 1 ns / 100 ps
2
3  //simpleALU
4  module simpleALU (A, B, Cin, Cntrl, O, Cout,segments);
5      input [3:0] A,B;
6      input [2:0] Cntrl;
7      input Cin;
8      output reg [3:0] O;
9      output reg Cout;
10     output reg [6:0] segments;
11
12     reg [3:0] Carry, Borrow;
13     always @ (*)
14     begin
15         case(Cntrl)
16             3'b000: begin //INC
17                 O = A + 1;
18                 if (A == 4'b1111)
19                     begin
20                         Cout = 1;
21                     end
22                 else
23                     begin
24                         Cout = 0;
25                     end
26             end
27             3'b001: begin //DEC
28                 O = A - 1;
29                 Cout = 0;
30             end
31             3'b010: begin //ROR
32                 O = {A[0],A[3],A[2],A[1]};
33                 Cout = 0;
34             end
35             3'b011: begin //SHR
36                 O = A >> 1;
37                 Cout = 0;
38             end
39             3'b100: begin //AND
40                 O = A & B;
41                 Cout = 0;
42             end
43             3'b101: begin //OR
44                 O = A | B;
45                 Cout = 0;
46             end
47             3'b110: begin //ADD
48                 O = A + B + Cin;
49                 Carry = (A && B) || ((A && Cin) || (B && Cin));
50                 Cout = Carry;
51             end
52             3'b111: begin //SUB
53                 O = A - B - Cin;
54                 Borrow = (!A && (B ^ Cin)) || (B && Cin);
55                 Cout = Borrow;
56             end
57         endcase

```


```

58     end
59
60     //7-Segment Display
61     always @ (0) begin
62         case (0)
63             0 : segments = 7'b0000001;
64             1 : segments = 7'b1001111;
65             2 : segments = 7'b0010010;
66             3 : segments = 7'b0000110;
67             4 : segments = 7'b1001100;
68             5 : segments = 7'b0100100;
69             6 : segments = 7'b0100000;
70             7 : segments = 7'b0001111;
71             8 : segments = 7'b0000000;
72             9 : segments = 7'b0000100;
73             10 : segments = 7'b0001000;
74             11 : segments = 7'b1100000;
75             12 : segments = 7'b0110001;
76             13 : segments = 7'b1000010;
77             14 : segments = 7'b0110000;
78             15 : segments = 7'b0111000;
79             default: segments = 7'b1111111;
80         endcase
81     end
82 endmodule
83
84 //simple ALU testbench
85 module simpleALU_tb;
86     parameter N = 32; //32 tests
87     reg [3:0] Atb,Btb;
88     reg [2:0] Sel;
89     reg Cintb;
90     wire [3:0] Otb;
91     wire Couttb;
92     wire [6:0] Segtb;
93
94     simpleALU U0 (
95         .A (Atb),
96         .B (Btb),
97         .Cin (Cintb),
98         .Cntrl (Sel),
99         .O (Otb),
100        .Cout (Couttb),
101        .segments (Segtb)
102    );
103
104     initial begin
105         $display("\t\ttime\tAtb,\tBtb,\tCintb,\tSel,\tOtb,\tCouttb,\tSegtb");
106         $monitor("%d,\t%b,\t%b,\t%b,\t%b,\t%b,\t%b", $time, Atb, Btb, Cintb, Sel, Otb, Couttb, Segtb);
107     end
108
109     integer i;
110     always begin
111         for (i = 0; i <= N; i = i + 1) begin
112             #10;
113             Atb = $random;
114             Btb = $random;
115             Cintb = $random;
116             Sel = $random;
117         end
118         $display ("\t\t\tTest Finished");
119         $stop;
120     end
121 endmodule
122

```

This is my Verilog code for the 4-bit ALU module testbench including the 7-segment output display.

C.

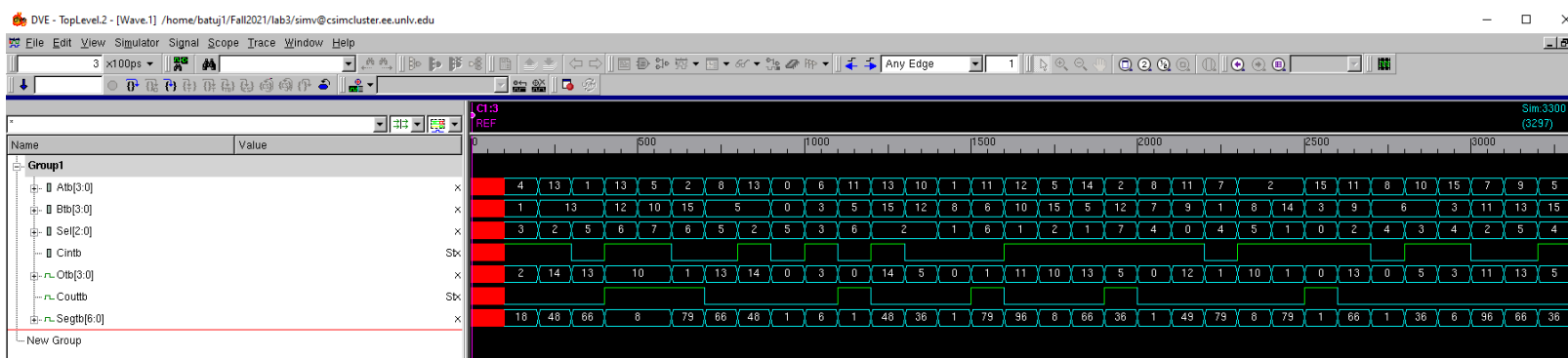

These are my waveforms from VCS that display the inputs and outputs of the 4-bit ALU testbench including the 7-segment output display. The blocks of red lines indicate delay.

```

Type: [Info] Severity: [Info] Code: All
Chronologic VCS simulator copyright 1991-2017
Contains Synopsys proprietary information.
Compiler version N-2017.12-SP2-14; Runtime version N-2017.12-SP2-14; Sep 18 11:53 2021
VCD+ Writer N-2017.12-SP2-14 Copyright (c) 1991-2017 by Synopsys Inc.
The file '/home/batuj1/Fall2021/lab3/inter.vpd' was opened successfully.

time  Atb,   Btb,   Cintb, Sel,   Otb,   Coutb, Segtb
0,    xxxx,  xxxx,  x,    xxx,  xxxx,  x,    xxxxxxx
10,   0100,  0001,  1,    011,  0010,  0,    0010010
20,   1101,  1101,  1,    010,  1110,  0,    0110000
30,   0001,  1101,  0,    101,  1101,  0,    1000010
40,   1101,  1100,  1,    110,  1010,  1,    0001000
50,   0101,  1010,  1,    111,  1010,  1,    0001000
60,   0010,  1111,  0,    110,  0001,  1,    1001111
70,   1000,  0101,  0,    101,  1101,  0,    1000010
80,   1101,  0101,  1,    010,  1110,  0,    0110000
90,   0000,  0000,  0,    101,  0000,  0,    0000001
100,  0110,  0011,  1,    011,  0011,  0,    0000110
110,  1011,  0101,  0,    110,  0000,  1,    0000001
120,  1101,  1111,  1,    010,  1110,  0,    0110000
130,  1010,  1100,  0,    010,  0101,  0,    0100100
140,  0001,  1000,  0,    001,  0000,  0,    0000001
150,  1011,  0110,  0,    110,  0001,  1,    1001111
160,  1100,  1010,  1,    001,  1011,  0,    1100000
170,  0101,  1111,  1,    010,  1010,  0,    0001000
180,  1110,  0101,  1,    001,  1101,  0,    1000010
190,  0010,  1100,  1,    111,  0101,  1,    0100100
200,  1000,  0111,  1,    100,  0000,  0,    0000001
210,  1011,  1001,  1,    000,  1100,  0,    0110001
220,  0111,  0001,  0,    100,  0001,  0,    1001111
230,  0010,  1000,  1,    101,  1010,  0,    0001000
240,  0010,  1110,  1,    001,  0001,  0,    1001111
250,  1111,  0011,  1,    000,  0000,  1,    0000001
260,  1011,  1001,  1,    010,  1101,  0,    1000010
270,  1000,  0110,  0,    100,  0000,  0,    0000001
280,  1010,  0110,  1,    011,  0101,  0,    0100100
290,  1111,  0011,  1,    100,  0011,  0,    0000110
300,  0111,  1011,  0,    010,  1011,  0,    1100000
310,  1001,  1101,  0,    101,  1101,  0,    1000010
320,  0101,  1111,  1,    100,  0101,  0,    0100100

Test Finished

```

This is my console output from VCS that displays the time for the test to finish, the inputs, and the outputs for the 4-bit ALU testbench including the 7-segment output display.

d.

https://drive.google.com/file/d/1ukPazOBCfBhTPD_-QSV45y_pNUsIS62B/view?usp=sharing

This is a link to my video displaying the opcode from the table for the 4-bit ALU. The video will also be included within the submission zip file.

4. Answers to questions

Question 1: What is an unintentional latch in a Verilog Design? Is it a good or bad design practice?

An unintentional latch in a Verilog Design is when the user inserts a latch in place of where combinational logic can be found. An example of this is when the user takes out the default case within a case statement. Instead of a multiplexer being formed, a latch would take its place because the net is not assigned to any known values. These unintentional latches may also occur from any missing signals within the sensitivity list. Unintentional latches are also called unintended latches or inferred latches. These unintentional latches are considered as bad design practice as the user is unintentionally creating these latches. By accidentally making these latches, the original design is altered; therefore, the user would need to go back into the Verilog code and rewrite it to where the combinational logic would form multiplexers.

Question 2: Why do we need a testbench? Is the waveform simulation not good enough?

We need a testbench to verify the functionality of a design and to report the inputs and outputs in a readable format within the console. The waveform simulation is only good enough in specific circumstances. By using a testbench, the user can check a large number of signals rather than by manually inputting them into the waveform simulation. In addition, the testbench, itself, can generate a periodic clock signal, acquire signal waveforms, and create a simulation report. Forcing inputs within a waveform simulation may be time consuming when there are multiple signals; hence, the testbench would make verification of functionality much quicker.

Question 3: Explain the differences between \$monitor and \$display.

\$monitor and \$display have several differences. \$monitor is a computing program for editing and viewing, whereas \$display is a screen that only shows graphics or text. \$display and \$write both display arguments in the order that they are laid out within the argument list. The key difference between the two is that \$display is used when values are to be printed to the console, and \$monitor is to be called only one time to print the value of a variable whenever it is to be altered. \$monitor is utilized to monitor signals when values change throughout the compilation of the Verilog code, and \$display is utilized every time to print values or display the immediate values of signals.

5. Conclusions & Summary

This lab was pretty straightforward as the lab instructions were somewhat clear. The only parts I did have confusion was for experiment 2 where the instructions said to create a Magnitude Comparator from prelab 2; however, this was a typo instead of prelab 2 it should've been prelab 3. The ripple adder was a great review because I remember doing a similar lab in CPE 200 L.

Experiment 1 seemed to have been carried over from CPE 200 L as the 7-segment display module is somewhat identical to the one in the previous class. Experiment 4 would probably be the most challenging as the 4-bit ALU implementation involved if statements within cases to include the cout within the outputs. I enjoyed reading upon testbenches as they were my struggle in the CPE 200 L class, and I am more comfortable with writing testbenches now than I was before. In addition, the hardest part of this lab was filming the video for the 4-bit ALU operations because the video took up a lot of data. Overall, I enjoyed this lab, and my knowledge of testbenches has increased as well as the implementation of our Verilog code into the DE2 board.